



PROCEDURE :- (A) Measurement of Armature resistance

1. Connect the circuit as per the circuit diagram.
2. At the time of switching ON the supply, the Variable DC supply must be in the minimum potential position.
3. Vary the DC supply and set the ammeter reading in 0.5A, at the time record the voltmeter reading
4. Repeat the step 3 and set the ammeter reading in 1 A, 1.5 A & 2 A.
5. Reduce the output voltage of DC supply in minimum position, and then switch OFF.

(B) Measurement of field resistance

1. Connect the circuit as per the circuit diagram.
2. At the time of switching ON the supply, the Variable DC supply must be in the minimum potential position.
3. Vary the DC supply and set the ammeter reading in 0.1A, at the time record the voltmeter reading.
4. Repeat the step 3 and set the ammeter reading in 0.15A, 0.2A & 0.25A
5. Reduce the output voltage of DC supply in minimum position then switch OFF.

OBSERVATION TABLE:-

(A) Measurement of Armature resistance

Sl.no	Voltage(V)	Current(I)	Resistance=V/I
		0.5A	
		1A	
		1.5A	
		2A	
Avg.=			

(B) Measurement of field resistance

Sl.no	Voltage(V)	Current(I)	Resistance=V/I
		0.1A	
		0.15A	
		0.2A	
		0.25A	
Avg.=			

CONCLUSION:-